

June 04

Additional Examination Questions - use as required.

Examiner  
only  
Arholwr  
yn unig

4. (a) A useful equation applying to a cell of e.m.f.  $E$  and internal resistance  $r$  is

$$V = E - Ir.$$

(i) State what is meant by the e.m.f. of the cell. [2]

.....  
.....



(ii) What does  $V$  represent? [1]

.....

(iii) What does  $Ir$  represent? [1]

.....

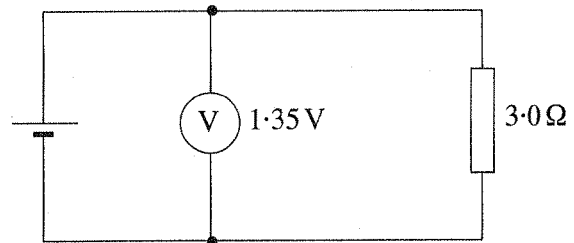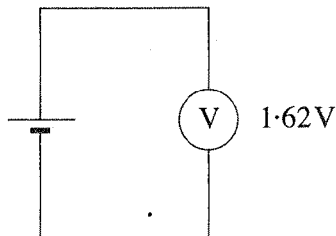(b) A voltmeter connected across the terminals of a cell reads 1.62 V. The reading drops to 1.35 V when a  $3.0\ \Omega$  resistor is connected in parallel with the voltmeter.



(i) (I) State the value of the e.m.f. of the cell. [1]

.....

(II) Calculate the cell's internal resistance. [2]

.....  
.....  
.....  
.....

- (ii) Calculate the rate, in watts, at which the cell's stored energy is converted when the resistor is connected. [2]

.....

.....

.....

- (iii) Calculate the power which is dissipated in the  $3.0\Omega$  resistor. [1]

.....

.....

.....

3. (a) A fixed potential difference of 6.0 V is applied across a coil of copper wire. At a temperature of 0°C the current through the coil is found to be 0.30 A. At 50°C the current is 0.24 A.

(i) Explain **in terms of electrons** why the current is smaller at 50°C than at 0°C. [3]

.....

.....

.....

.....

.....

(ii) Calculate the temperature coefficient of resistance of copper. [4]

.....

.....


.....

.....

.....

.....

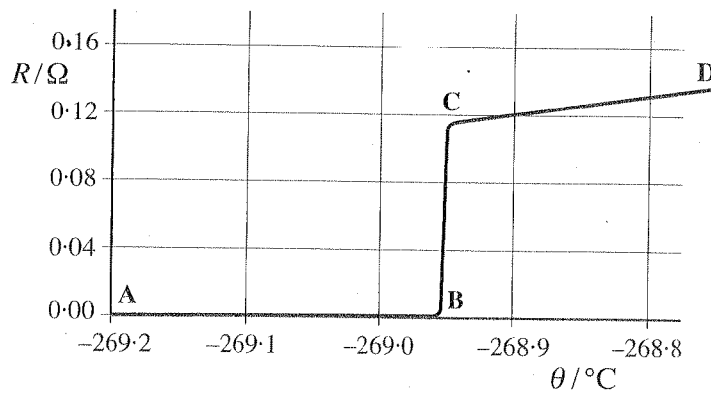(b) In 1911 a Dutch physicist was investigating the effects of very low temperatures. He plotted a graph (see below) of the measured resistance,  $R$ , of a solid mercury specimen against temperature,  $\theta$ .



(i) What name do we now give to the effect responsible for the region AB? [1]

.....

(ii) What potential difference would be needed to **maintain** a current of (say) 10 mA in a ring of solid mercury at a temperature of -269.0°C or lower? [1]


.....

(iii) No 'points' were obtained for the region BC. Suggest a reason for this. [1]

.....

.....

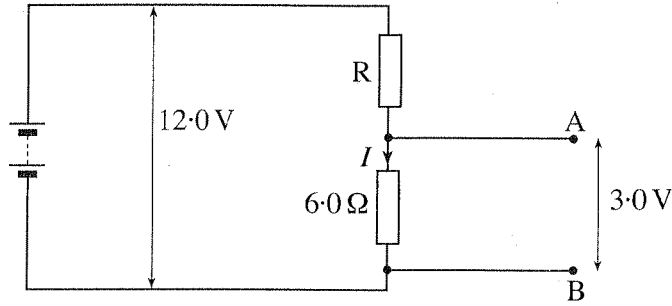4. (a) The diagram shows two resistors connected in a series across a 12.0 V supply to give an 'output' of 3.0 V. [The supply has negligible internal resistance.]




- (i) What is the name for a resistor combination used in this way? [1]

- (ii) Calculate the current,  $I$ . [1]

- (iii) State the potential difference across the resistor  $R$ . [1]

- (iv) Calculate the resistance of  $R$ . [2]

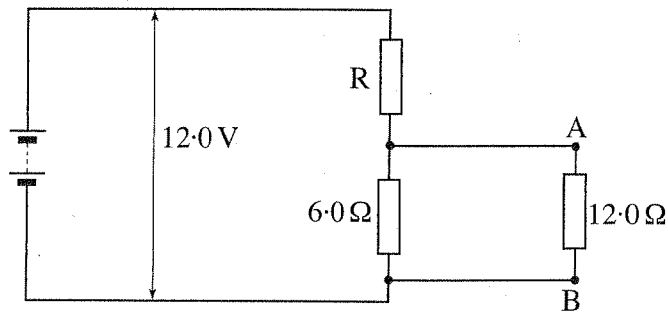- (b) A 12.0 Ω 'load' resistor is now connected across the output terminals, A and B, as shown.




- (i) Calculate the resistance of the parallel combination of 6.0 Ω and 12.0 Ω resistors. [2]

- (ii) Calculate the current through resistor  $R$ . [2]

- (iii) Calculate the new potential difference between A and B. [1]

Jan'03

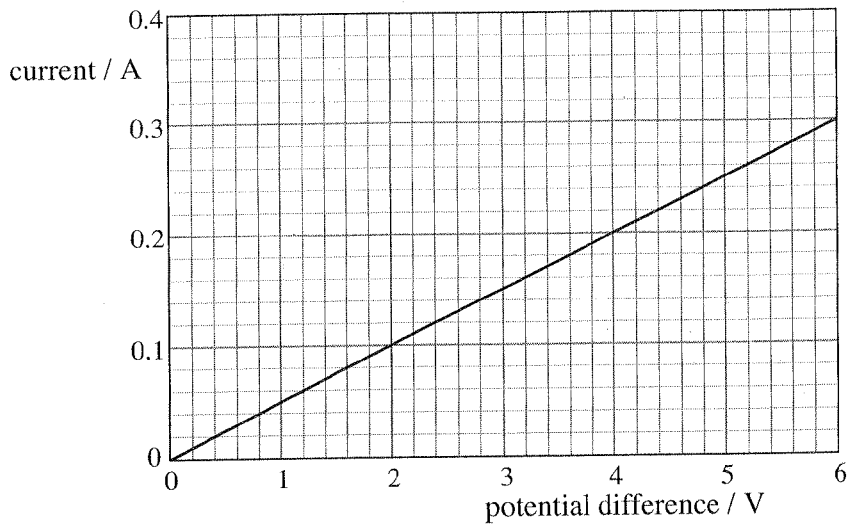6. (a) A graph of current against applied potential difference is given for a piece of alloy wire.



(i) Draw a circuit diagram of an arrangement that could have been used to obtain the readings. Show the alloy wire as a resistor labelled 'W'. [3]

(ii) Calculate the resistance of the wire. [1]

.....  
.....  
.....

(iii) Calculate the current in the wire if a potential difference of 14 V were applied, stating any assumption you are making. [2]

.....  
.....  
.....

(iv) The wire has a length of 8.0 m and a **diameter** of  $2.5 \times 10^{-4}$  m. Calculate

(I) its cross-sectional area, [2]

.....  
.....  
.....

(II) the resistivity of the alloy. [3]

.....

.....

.....

.....

(v) Draw on the same graph-grid (facing page) the current against voltage graphs for

(I) a wire, made of the same alloy, of diameter  $2.5 \times 10^{-4}$  m and length 24 m.  
[Label this graph 'I'] [1]

(II) a wire, made of the same alloy, of diameter  $5.0 \times 10^{-4}$  m and length 8.0 m.  
[Label this graph 'II'] [2]

(b) The current in a metal wire of cross-sectional area  $A$  is given by the formula


$$I = nAve$$

(i) State the meanings of  $n$  and of  $v$ . [2]

$n$ : .....

$v$ : .....

(ii)

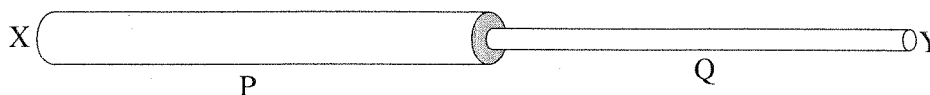

Two copper wires, P and Q, are connected in series. P has 10 times the cross-sectional area of Q. A battery is connected between the ends, X and Y, of the combination.

(I) List the quantities in the equation above which have the same value in both P and Q. [2]

.....

(II) Deduce how the value of  $v$  in P compares with the value of  $v$  in Q, explaining your reasoning. [2]

.....

.....

.....

.....

Turn over.

Jan 03

2. (a) Explain what is meant by the *e.m.f.* of a battery. [2]

.....

.....

.....

- (b) Three cells, **each** of e.m.f. 1.5 V and internal resistance 0.50  $\Omega$ , are connected in series to make a battery of e.m.f. 4.5 V. The battery is connected to a resistor, R, of resistance 6.0  $\Omega$ .

- (i) Sketch a circuit diagram. Include the internal resistance, and label it. [1]

- (ii) Calculate the current through the circuit. [2]

.....

.....

.....

.....

- (iii) Calculate the potential difference across the resistor, R. [2]

.....

.....

.....

.....

- (iv) Suppose that one of the cells had been connected the wrong way round. Calculate the current in the circuit in this case. [3]

.....

.....

.....

.....

.....

7. (a) Define the *e.m.f.* of a cell.

[2]

.....

.....

(b) A car battery consists of six cells, **each** of *e.m.f.* 2.0 V and internal resistance 0.0020 Ω, connected in series.

(i) Write down the internal resistance of the car battery.

[1]

.....

(ii) To start the car, a 'starter-motor' is connected to the battery. A current of 180 A flows through the battery and the motor. Calculate the *p.d.* across the battery terminals for this current.

[3]

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(iii) When doing repairs under the bonnet of a car, it may be safest to remove the battery to prevent accidental short-circuits. Suppose a spanner were to be dropped and came to rest bridging the battery terminals. The spanner can be taken to have no resistance.

(I) How large would the current be?

[2]

.....

.....

.....

.....

(II) Calculate the *power* produced by the battery.

[2]

.....

.....

(III) Give a reason why such an accident could be very dangerous.

[1]

.....

.....

(c) Suppose the battery in your car is 'flat' (has run out of energy).

- (i) A friend (who has not studied AS level Physics) suggests that the battery could be replaced by a **number of** cells of the type used in torches, connected in series. Each cell has an e.m.f. of 1.5 V and an internal resistance of 0.30  $\Omega$ . Explain why the **maximum** current such an arrangement could possibly supply is 5.0 A, no matter how many cells are used. [2]

.....

.....

.....

.....

- (ii) A better idea for starting the car is to use a pair of insulated copper wires (called 'jump-leads') to connect to a battery in a friend's car. Suppose that **each** wire is 3.0 m long and that the voltage drop along **each** wire is 0.72 V for a current of 180 A. The resistivity of copper is  $1.7 \times 10^{-8} \Omega\text{m}$ .

- (I) Calculate the cross-sectional area of the wire. [3]

.....

.....

.....

.....

.....

- (II) Hence calculate the **diameter** of the wire. [2]

.....

.....

.....

- (III) Discuss whether, ideally, jump leads should be made of wire of larger or smaller diameter. [2]

.....

.....

.....


Jan 04

2. (a) In a Physics practical class a teacher gives a student a sealed box with **two** terminals, containing a combination of two resistors. One has a known value of  $10\ \Omega$  and the other has an unknown resistance,  $X$ . The student finds that when a p.d. of  $15\ \text{V}$  is placed across the terminals, a current of  $2.5\ \text{A}$  flows through the combination.

(i) Calculate the resistance of the combination. [1]

(ii) Explain why the resistors cannot possibly be in series. [1]

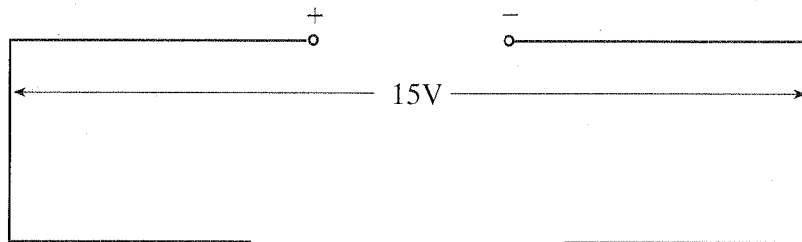(iii) Add the resistor combination to complete the circuit diagram below. [1]



(iv) For the same p.d. of  $15\ \text{V}$ , calculate the current in  
(I) the  $10\ \Omega$  resistor, [1]

(II) the other resistor. [1]

(v) **Hence** calculate the resistance  $X$ , of this other resistor. [1]

(vi) Use the appropriate resistance combination formula to check whether your answers to (i) and (v) are consistent with each other. Show your method clearly. [2]

.....

.....

.....

.....

.....


(b) Which step in part (a) relies directly on the conservation of charge? Briefly explain your answer. [2]

.....

.....

June 04

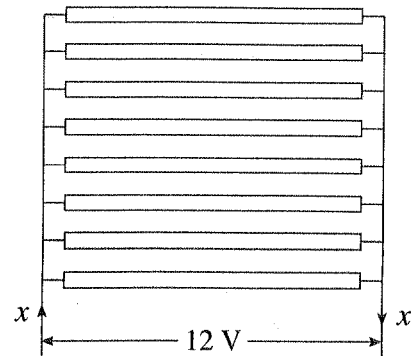1. A rear-window heater for a car consists of 8 strips of copper, bonded to the glass and connected in parallel, as shown. Each strip has a resistance of  $5.0\ \Omega$ .



(a) A potential difference of 12 V is applied across the combination. Calculate

(i) the current through each strip, [1]

.....  
.....

(ii) the current,  $x$ , through the combination, [1]

.....  
.....

(iii) the resistance of the combination. [1]

.....  
.....

(b) If the strips were to be connected *in series* the current,  $y$ , would be too small to give a useful heating effect. Calculate the ratio  $x/y$ . [2]

.....  
.....  
.....

(c) Each strip of copper is 1.1 m long and the resistivity of copper is  $1.7 \times 10^{-8}\ \Omega\text{m}$ .

(i) Calculate the cross-sectional area of a strip. [3]

.....  
.....  
.....  
.....


(ii) Each strip is 1.5 mm wide and its thickness is uniform. Calculate this thickness. [2]

.....  
.....  
.....

3. (a) State Ohm's Law.

[2]

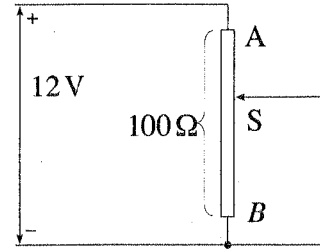(b) The diagram shows a variable potential divider consisting of a carbon track, AB, of resistance  $100\ \Omega$ . An 'input' of  $12.0\ \text{V}$  is applied across AB. The sliding contact, S, is positioned so that the p.d. between S and B is  $8.4\ \text{V}$ .



Calculate


(i) the resistance of the carbon track between S and B,

[2]

(ii) the p.d. between A and S.

[1]

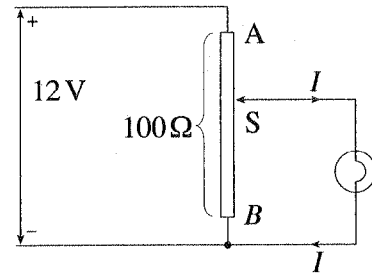(c) A filament lamp is now connected between S and B in the circuit of part (b). S remains in the same position. A current,  $I$ , flows through the lamp, as shown. State, **with reasons**, whether the following quantities increase, decrease, or stay the same when the lamp is connected:



(i) the current through the track between A and S;

[2]

(ii) the p.d. between A and S;

[1]

(iii) the p.d. between S and B.

[2]